

Growth of current in L-R circuit (Helmholtz Equation)

Consider a circuit having an inductance L and a resistance R placed in series with a battery of emf E as shown in fig(1)

When the key K is in position 1, the current slowly increases from zero to a maximum value I_0 after sometime.

During the time the current is growing there is a back emf in the inductance.


Let I be the value of the current at any instant during the variable state and $\frac{dI}{dt}$ be the rate at which the current grows,

then

$$\text{Fall of potential across the resistance} = RI$$

Back emf in the inductance

$$= -L \frac{dI}{dt}$$

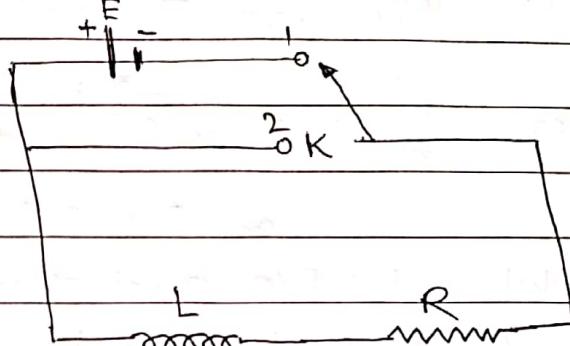

Since Back emf opposes the emf E due to the battery. Thus with two sets of emf the net emf is $E - L \frac{dI}{dt}$.

Applying Kirchhoff's 2nd Law (or voltage Law)

Now gives the loop equation as

$$\left[E - L \frac{dI}{dt} \right] = RI$$

Dividing both side by R , we have

$$\frac{E}{R} - L \frac{dI}{R dt} = I$$

$$\text{or } \frac{E}{R} - I = \frac{L}{R} \frac{dI}{dt} \quad \text{Dividing both sides by } dI$$

$$\text{and taking the reciprocals, we have } \frac{dI}{E/R - I} = \frac{R}{L} dt$$

Teacher's Signature: _____

$$\text{or } \frac{-dI}{\frac{E}{R} - I} = \frac{R}{L} dt$$

Integrating both sides, we have

$$\log_e \left(\frac{E}{R} - I \right) = -\frac{R}{L} t + C \quad (1)$$

where C is constant of integration

When $t=0$, Substituting these values in eqn (1), we have

$$\log_e \left(\frac{E}{R} \right) = C \quad \therefore \log_e \left(\frac{E}{R} - I \right) = \log_e \left(\frac{E}{R} \right) - \frac{R}{L} t$$

$$\text{or } \log_e \frac{\frac{E}{R} - I}{\frac{E}{R}} = -\frac{R}{L} t \quad \text{or } \frac{\frac{E}{R} - I}{\frac{E}{R}} = e^{-\frac{R}{L} t}$$

$$\text{or } \frac{E}{R} - I = \frac{E}{R} e^{-\frac{R}{L} t} \quad \text{or } I = \frac{E}{R} (1 - e^{-\frac{R}{L} t}) \quad (2)$$

$$\text{or } I = I_0 (1 - e^{-\frac{R}{L} t}) \quad (3)$$

where $I_0 = E/R$ gives final steady value of the current
eqn (3) gives the growth of current in L-R circuit.

Conclusion: (i) At $t=0$, $I=0$

(ii) As t increases, the 2nd term decreases and hence current increases exponentially.

(iii) At $t \rightarrow \infty$, the current tends to steady state value $I_0 = E/R$.

The curve of current I against t is

Time constant: The fraction $\frac{L}{R}$ is called the time constant of the circuit


If $t = \frac{L}{R}$, then

$$I = I_0 (1 - e^{-\frac{t}{\frac{L}{R}}}) = I_0 (1 - e^{-\frac{R}{L} t})$$

$$= I_0 \left(1 - \frac{1}{e} \right) = I_0 \left(\frac{e-1}{e} \right)$$

$$= I_0 \left(\frac{1.718}{2.718} \right)$$


$$\therefore I = 0.632 I_0$$

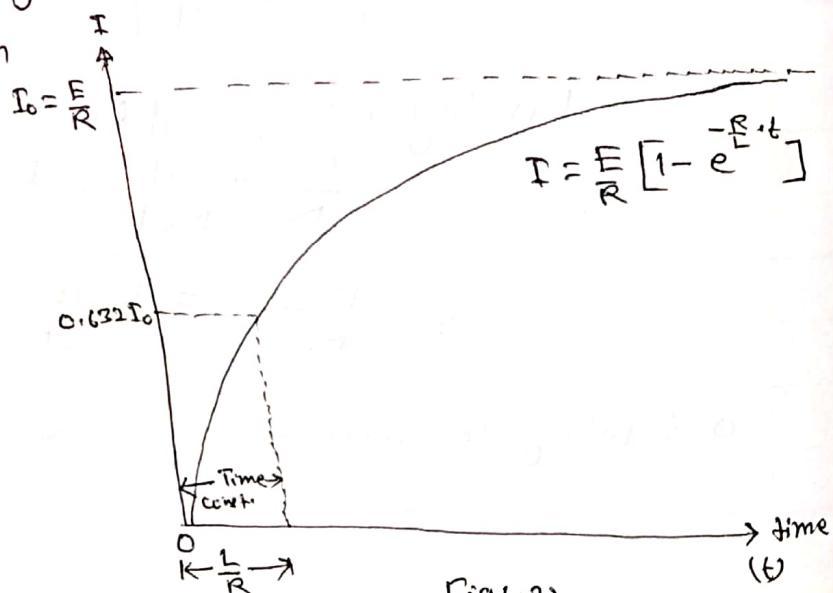

Hence time constant of LR circuit is defined as time during which the current rises to be 63.2%

Decay of current in L-R circuit

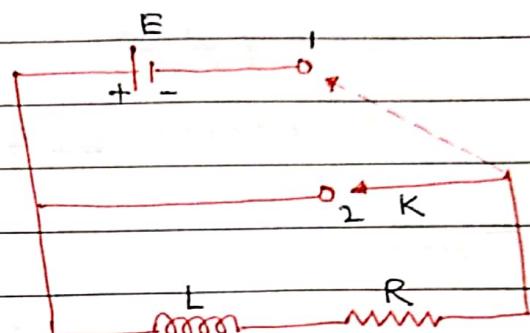After the steady current has been established, the source of steady emf is now removed and connecting to position 2, the current begins to decay (fall) exponentially in L-R circuit as shown in Fig (2).



During the time the current is decreasing, there is an emf induced in the inductance having a value $e = -L \frac{dI}{dt}$. The differential loop equation using Kirchhoff's 2nd Law is

$$\left[0 - L \frac{dI}{dt} \right] = RI$$

$$\text{or } \frac{dI}{I} = -\frac{R}{L} t \quad \text{Integrating both sides, we get}$$

$$\int \frac{dI}{I} = -\frac{R}{L} \int dt + B$$

where B is a constant of integration.

$$\therefore \log_e I = -\frac{R}{L} t + B \quad \text{--- (4)}$$

When $t = 0$, then $I = I_0$

$$\therefore \log_e I_0 = 0 + B \quad \text{or } B = \log_e I_0$$

Substituting for B in eqn (4), we get

$$\log_e I = -\frac{R}{L} t + \log_e I_0$$

$$\text{or } \log_e I - \log_e I_0 = -\frac{R}{L} t$$

$$\text{or } \log_e \left(\frac{I}{I_0} \right) = -\frac{R}{L} t$$

$$\text{or } \frac{I}{I_0} = e^{-\frac{R}{L} t} \quad \text{or } I = I_0 e^{-\frac{R}{L} t} \quad \text{--- (5)}$$

Thus, the current decays exponentially from its maximum value ($I_0 = \frac{E}{R}$) to zero

Teacher's Signature: _____

putting $\frac{L}{R} = t$ (Ineqns)

we have

$$I = I_0 e^{-\frac{t}{\tau}} = \frac{I_0}{e} \quad (6)$$

$$= I_0 \left(\frac{1}{e^{t/\tau}} \right)$$

$$= 0.367 I_0 \quad (7)$$

Time constant :

Time constant of

$$LR \text{ circuit} = \frac{L}{R}$$

The dimension of L are $\frac{\text{Volt}}{\text{Amp}} = \frac{\text{V.s}}{\text{A}}$

and dimension of R are $\frac{\text{Volt}}{\text{amp}}$

$$\therefore \text{Dimension of } \frac{L}{R} = \frac{\text{Volt.sec}}{\text{amp}} \times \frac{\text{amp}}{\text{volt}} \\ = \text{sec} [T]$$

The time constant of LR circuit may be defined as the time during which the current falls to $\frac{1}{e}$ of its maximum value

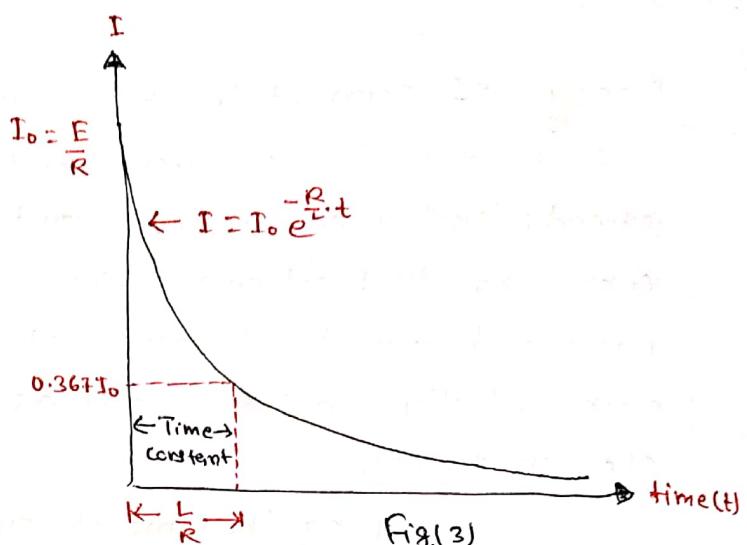


Fig.(3)

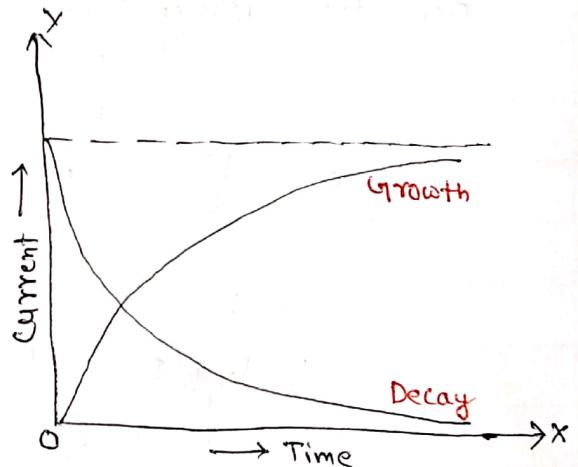


Fig.(4)